

इरिसेट

BLOCK SIGNALLING LABORATORY ब्लॉक सिगनलिंग प्रयोगशाला

प्रयोग सं. बी एस एल - 05

EXPERIMENT NO.: BSL. - 05

IRISET

नाम						
	:					
अनुक्रमांक				प्राप्तांक		
Roll No	:			Marks Awarded	:	
पाठ्यक्रम						
	:					
दिनांक				अनुदेशक के आदक्षर		
Date	:			Instructor's Initial	:	
a) Don't	of Oi	ne Line Clear – O Line Clear, but	ne Train principl	LEAR -ONE TRAIN For and the essentials of SS. Is it possible to take	f Absolute Blo	Yes/No
			ake OFF LSS. Pos	the Block section and	record	Yes/No
*		-	as the train enters nd try to take OFF		record	
,		ble to take OFF I	•	Loo agam.		Yes/No
				_ position at Receiving	g End.	
f) Now		_ relay is energis	ed at the sending	end and the Block han	dle is locked in	l
				be taken OFF at sendi		
				Line Clear contact of		
_				S of dispatching end of		
				position position bring the Block hand		
			it possible to norr			Not possible
		-	-	gnal knob and try to b		-
		osition to Line C		, <i></i>		ot possible
	•		•			•
entered in Even thou	nto th ugh t	e Block section,	the stick feed to _s indicating Line	ause relay is c relay is cut off Clear, it is not possible	f.	
receiving	stati iple o	on. Now, the Li	ne Clear for the	released only after next train can be grand achieved in the design	nted. With the	ese features,

II.	Trouble	shooting	on Double	Line	Block	Instruments:
			OII D OUNIC			TILDUI GILLUITO

a) Disconnect the +ve bell supply X+ wire at Bell spring assembly at Stn.A

Press bell plunger at Stn.A. Whether bell beat is received at Stn.B?

Yes/No

Restore the wire connection at Stn.A

b) Disconnect the wire X of bell relay at bell spring assembly at Stn.B

Press bell plunger at Stn.A. Whether bell beat is received at Stn.B?

Yes/No

Restore the wire connection at Stn.A

c) Disconnect the +ve supply wire of indication battery at Stn.A

Turn the Commutator handle at Stn.A to Line Clear and observe whether the bottom indicator at Stn.A and Top indictor at Stn.B display Line Clear Yes/No

Restore the wire connection at Stn. A

d) Disconnect the wire of Polarised relay R2 terminal at Stn.B

Turn the Commutator handle at Stn.A to Line Clear and observe whether the bottom indicator at Stn.A and Top indictor at Stn. B display Line Clear Yes/No

Restore the wire connection at Stn.B

e) Disconnect the wire at terminal BL2 at Stn.A

Turn the Commutator handle at Stn.A to Line Clear and observe whether the bottom indicator at Stn.A and Top indictor at Stn.B display Line Clear

Yes/No

Restore the wire connection at Stn.A

f) Disconnect the wire at terminal BL1 at Stn.B

Turn the Commutator handle at Station A to Line Clear, whether the bottom indicator at Stn.A and Top indictor at Stn.B display Line Clear

Yes/No

Restore the wire connection at Stn.B.

Signature of Trainee